

# Electronics for Pedestrians

Ralph J. Steinhagen, CERN

– Tutorial I/II –

*“In theory, 'theory' and 'praxis' are the same, in praxis they aren't”*

# Quick getting started with Qucs

- QUCS – Quite universal circuit simulator:  
<http://qucs.sourceforge.net/>

- similar to Spice™ & derivatives but open-source
- DC, AC, S-parameter, harmonic balance analysis, noise analysis, RF structures, etc.




- If you haven't it already: Linux, Mac & Windows version available at:  
<http://qucs.sourceforge.net/download.html>
  - Linux: install from your favourite repository, we use version 0.0.17 but earlier should work as well.
  - Mac: you may need the following steps to temporarily disable security settings:  
<http://osxdaily.com/2012/07/27/app-cant-be-opened-because-it-is-from-an-unidentified-developer/>
  - Windows installation (+ dependent packages) should be straight forward

# Quick getting started with Qucs

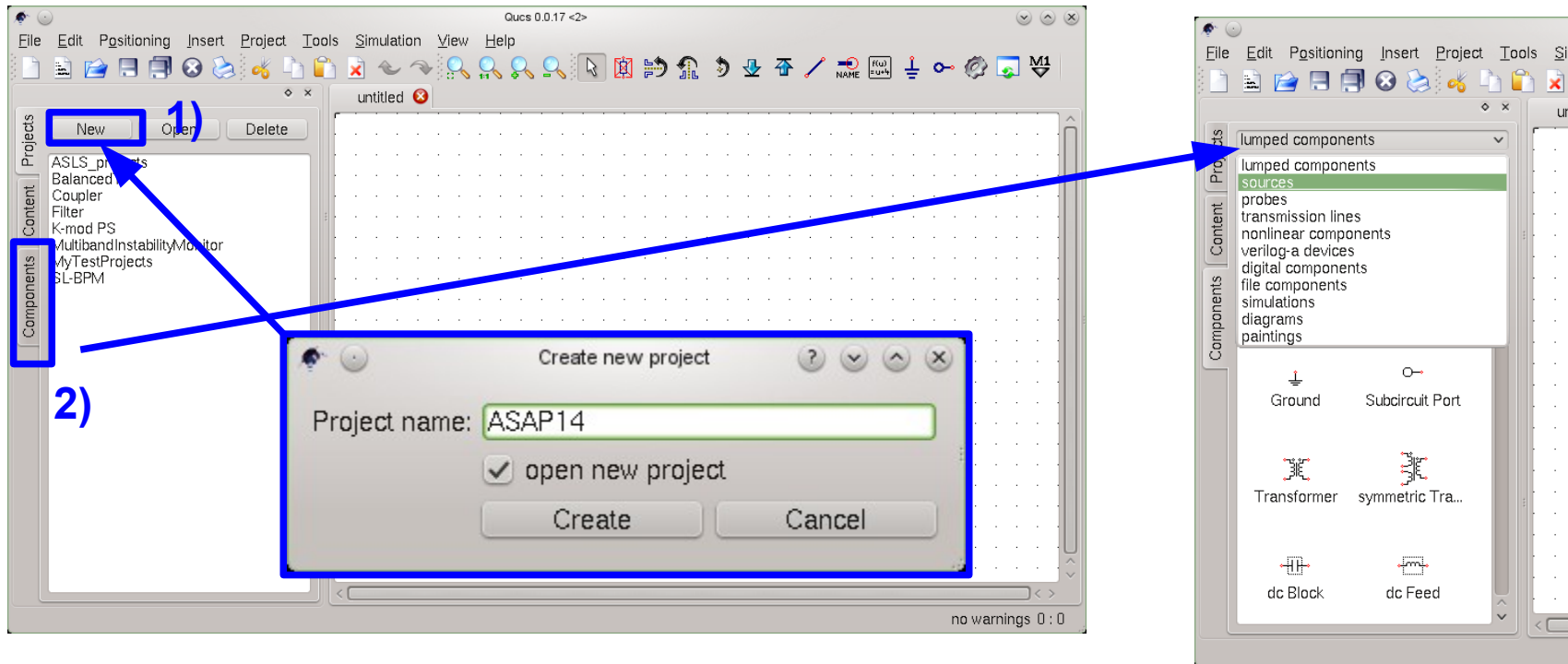1) Project → New Project → *<type and confirm project name>*

- This creates a new projects and switches to '**Content**' tab




2) Now you can start editing your schematic. The available components can be found in the '**components**' tab.

- there is a sub-menu for different categories of components  
→ feel free and encouraged to browse
- more precise parts and pre-configured elements can be found in:  
Tools → 'Component Library' (or via 'Ctrl + 4')
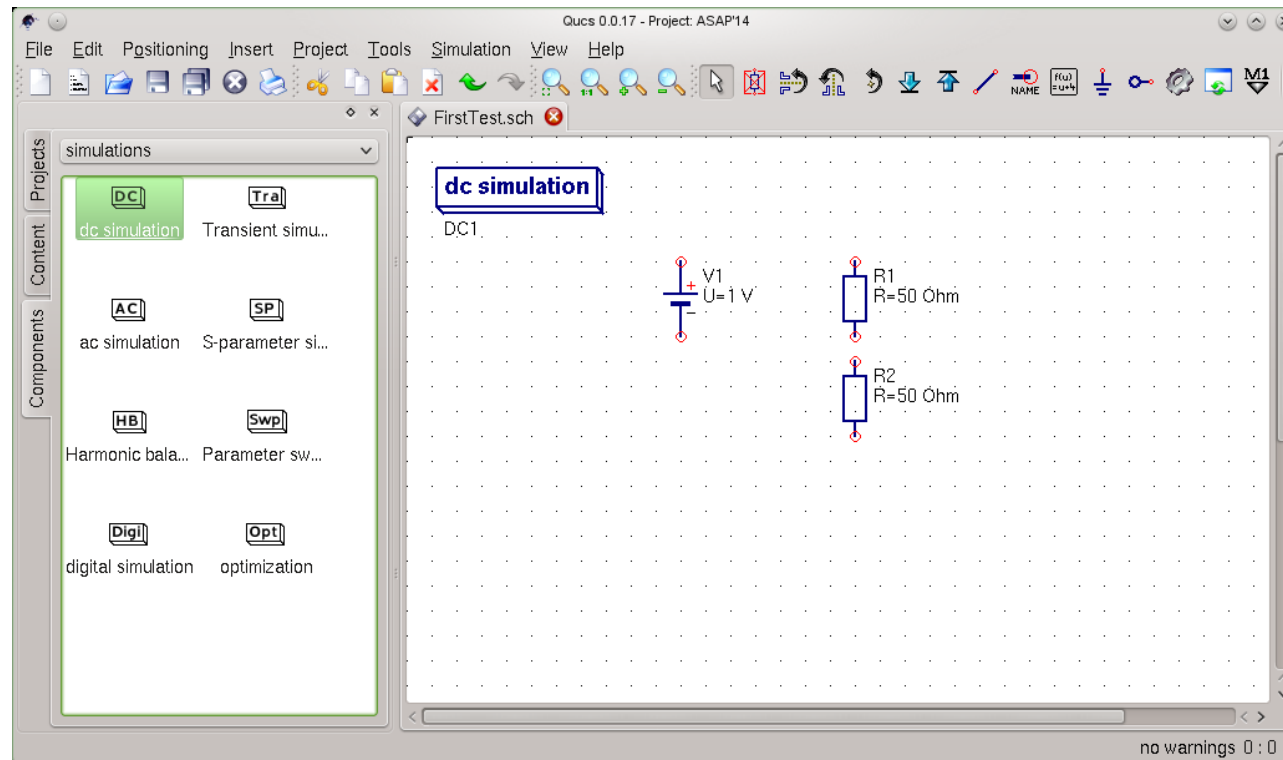
# Quick getting started with Qucs


Design and simulate a simple voltage divider:

- Place two resistors (i.e. drag-and drop) onto the schematic:  
*Components* → *lumped components* → *resistor*
  - N.B. You can rotate the components via 'Ctrl+R'
- Place a dc voltage onto the schematic:  
*Components* → *sources* → *dc Voltage Source*



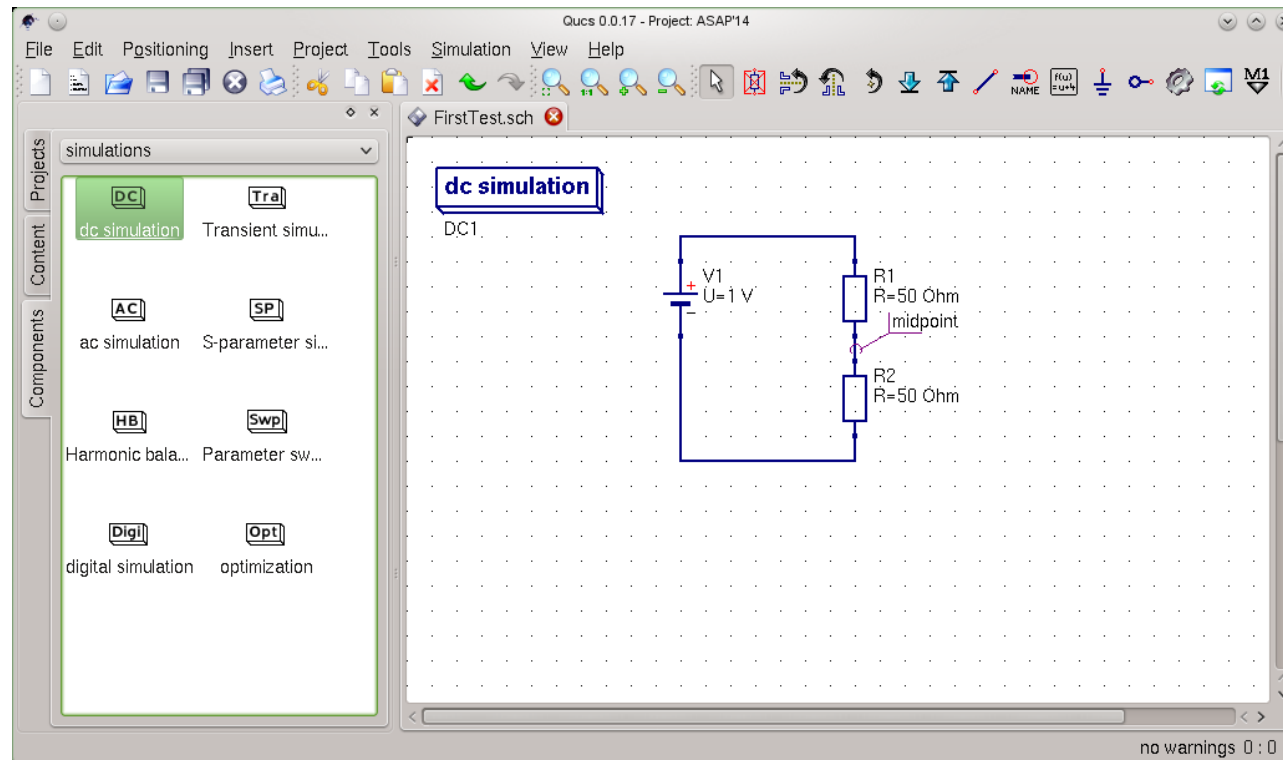
# Quick getting started with Qucs

- Wire the parts either using the 'wire' button, or 'Ctrl+E')
- Place a simulation block – in our case 'DC':  
*Components* → *simulations* → *dc simulation*
- Label wires to calculate voltages of give nodes:  
*Insert* → *Wire Label* (or 'Ctrl+L') – <type/confirm name>
- N.B. if you haven't already → save the schematic:  
*File* → *Save (as)* (or 'Ctrl+S') → <type descriptive name>


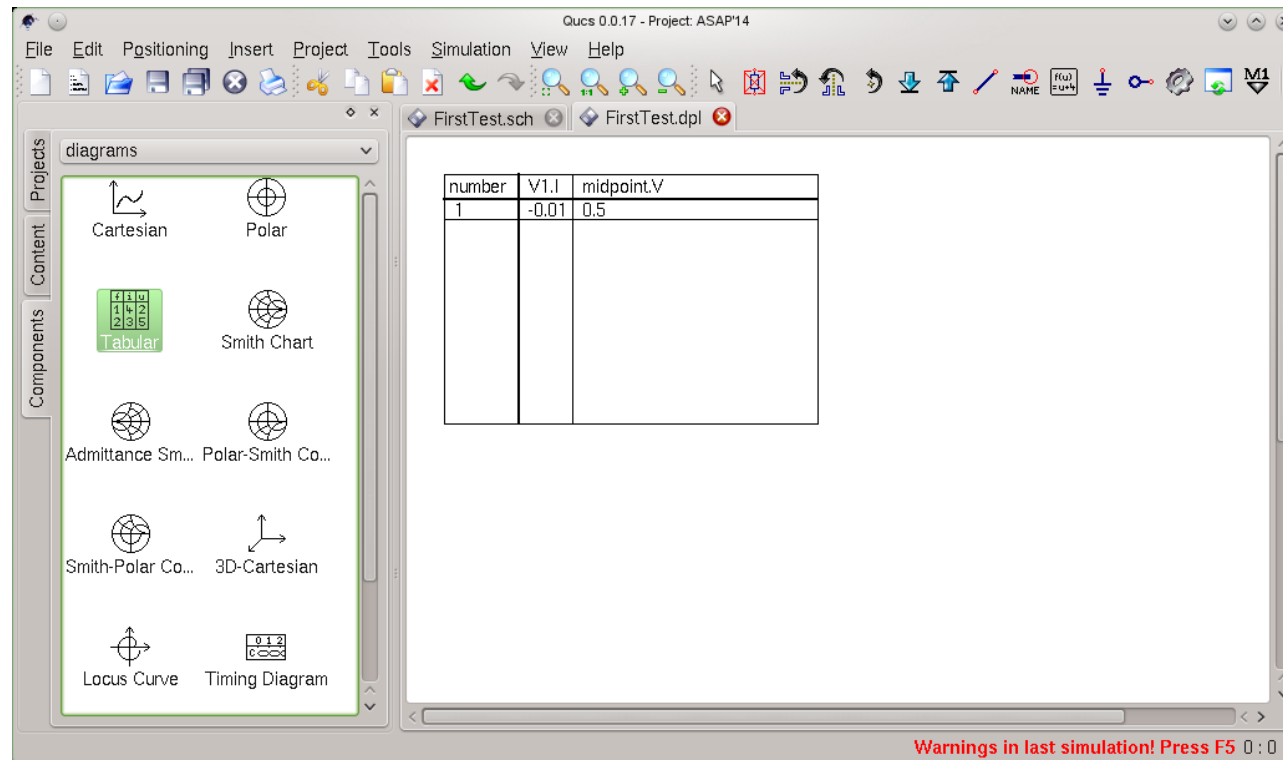
# Quick getting started with Qucs

- Issue a Simulation: *Simulation* → *Simulate* (or 'F2')
  - This opens a new panel (<name>.dpl) which can house the results and opens the 'Components→diagrams' sub-panel on the left (you can switch back and forth with 'F4') (you may change this via 'File → Document Settings → 'open data display ...' check-box)
- You can add e.g. a table and select (double-click) the nodes for which the currents and voltages have been calculated (here: 'V1.I' & 'midpoint.V')



# Quick getting started with QuCS

---

## Available dataset items

- Depending on the type of simulation performed you find the following types of items in the dataset:
  - *node.V* – DC voltage at node *node*
  - *name.I* – DC current through component *name*
  - *node.v* – AC voltage at node *node*
  - *name.i* – AC current through component *name*
  - *node.vn* – AC noise voltage at node *node*
  - *name.in* – AC noise current through component *name*
  - *node.Vt* – transient voltage at node *node*
  - *name.It* – transient current through component *name*
  - *S[1,1]* – S-parameter value
- N.B. Please note that all voltages and currents are peak values and all noise voltages are RMS values at 1Hz bandwidth

# Quick getting started with QuCs

- Additional functions:
  - read & write data to file
  - execute octave (matlab) scripts
  - (simple) equations
  - ... extend missing functionality (i.e. it's open-source)

- Equations:

- ... = PlotVs(<variable a>, <variable b>, ...)
- ... = dB(<variable a>) or ... = a\*b
- ... = Time2Freq(<variable y>, <time vector>)
- variables/component value definition → useful if you e.g. want to test two scenarios – just disable ('Ctrl+D') the equation set that isn't in use

- More detailed info:

- Help → Tutorials → Equations.pdf
- Help → Tutorials → Functions.pdf



Equation

```
Eqn1
lc=-V1.l
beta=lc/lbase
beta_vs_lc=PlotVs(beta,lc)
```

Equation

```
Eqn1
transmission=dB(S[2,1])
phase=phase(S[2,1])
```

Equation

```
Eqn1
Spectrum_Input=dB(Time2Freq(Vin.Vt, time))
Spectrum_Vdet=dB(Time2Freq(Vdet.Vt, time))
Spectrum_Vout=dB(Time2Freq(Vspectrumanalyser.Vt, time))
Spectrum_Vac=dB(Time2Freq(Vout.Vt, time))
```

Equation

```
Cs=10e-6
R1=40e3
R2=10e3
Rc=1000
Re=100
Ce=10e-6
```

Ctrl+D

~~Equation~~



```
Cs=10e-6
R1=40e3
R2=10e3
Rc=1000
Re=100
Ce=10e-6
```


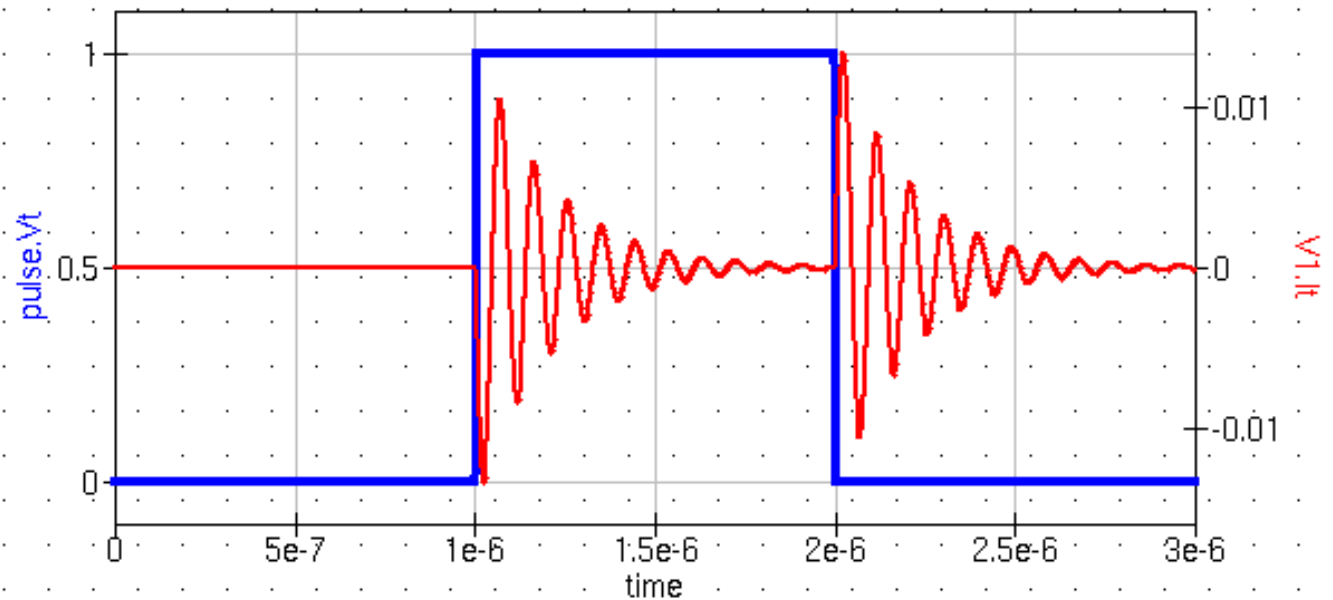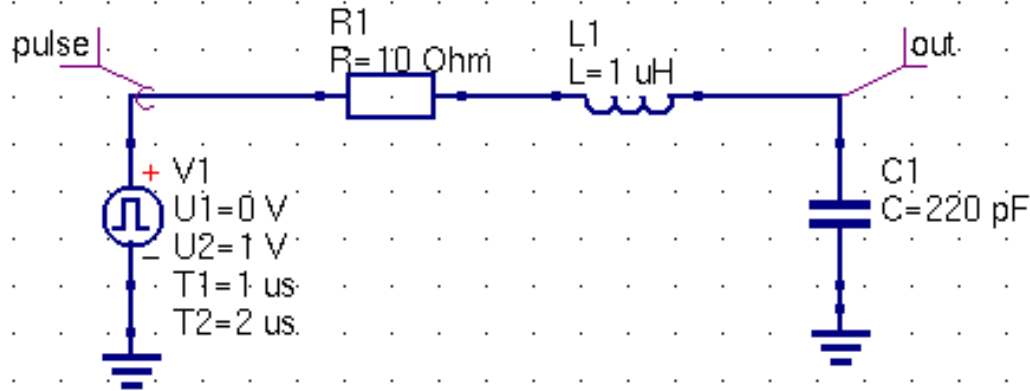
# Qucs – Resonant Circuit


transient simulation

TR1  
Type=lin  
Start=0  
Stop=3 us  
Points=1001



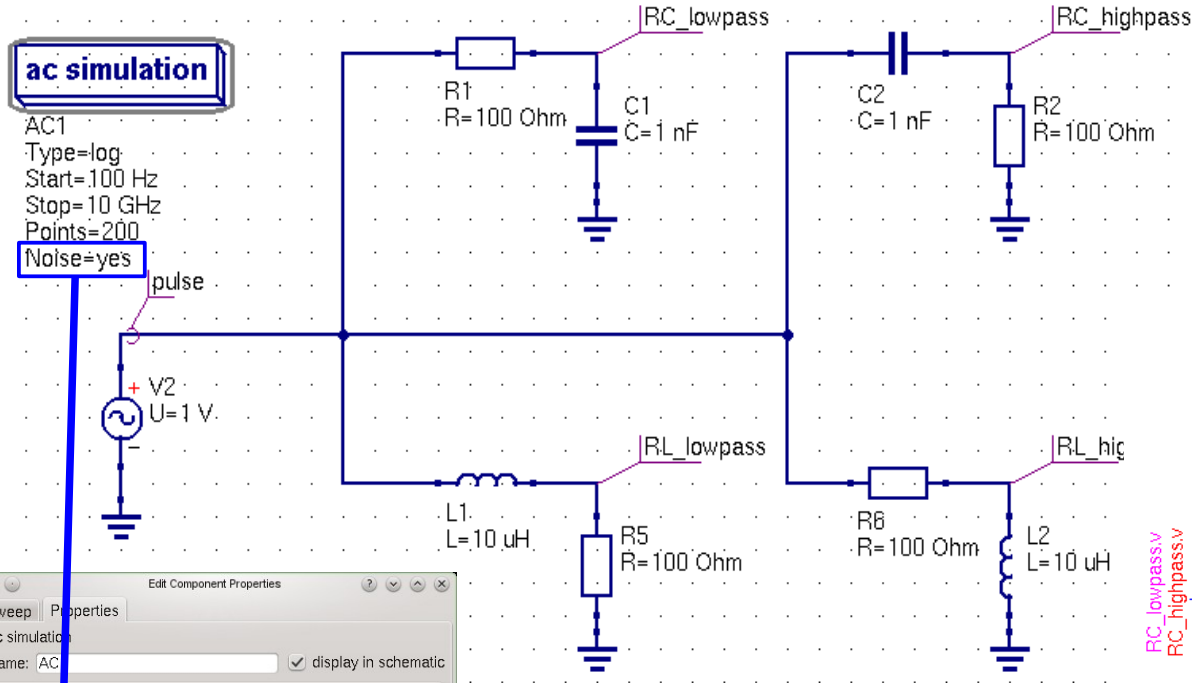
# Qucs – AC Simulation

- ... going to be used more frequently during RF tutorial
  - N.B. Noise simulation needs to be manually enabled:  
ac simulations → 'Properties' tab → Noise = <yes/no> (optional: 'display in schematic')



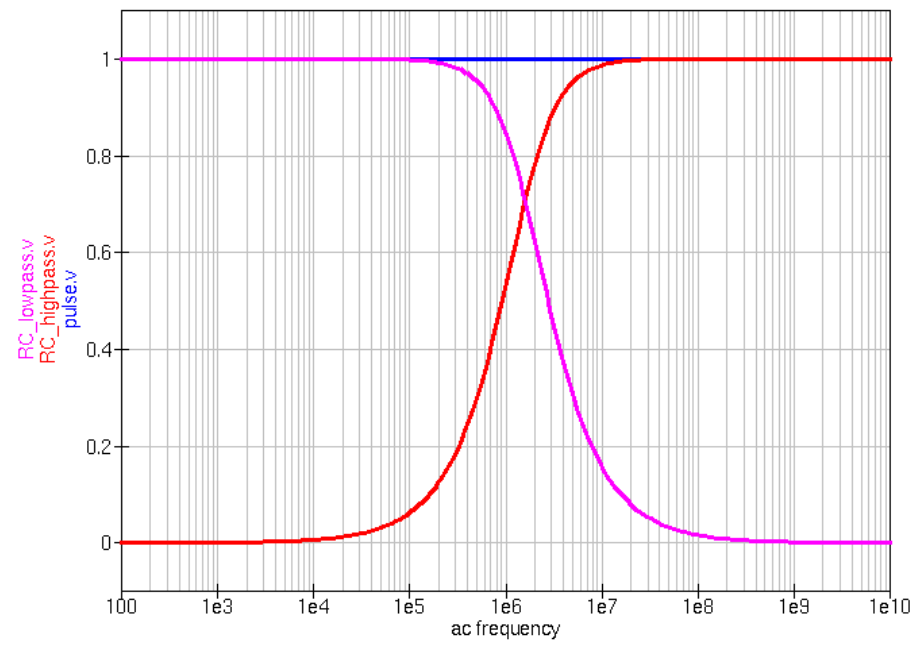**ac simulation**

AC1  
Type=log  
Start=100 Hz  
Stop=10 GHz  
Points=200  
Noise=yes



Edit Component Properties

Sweep Properties  
ac simulation  
Name: AC1  display in schematic


Name	value	display	Descri	Noise
Noise	yes	yes	calculate	calculate noise voltages [yes, no] yes

display in schematic

OK Apply Cancel
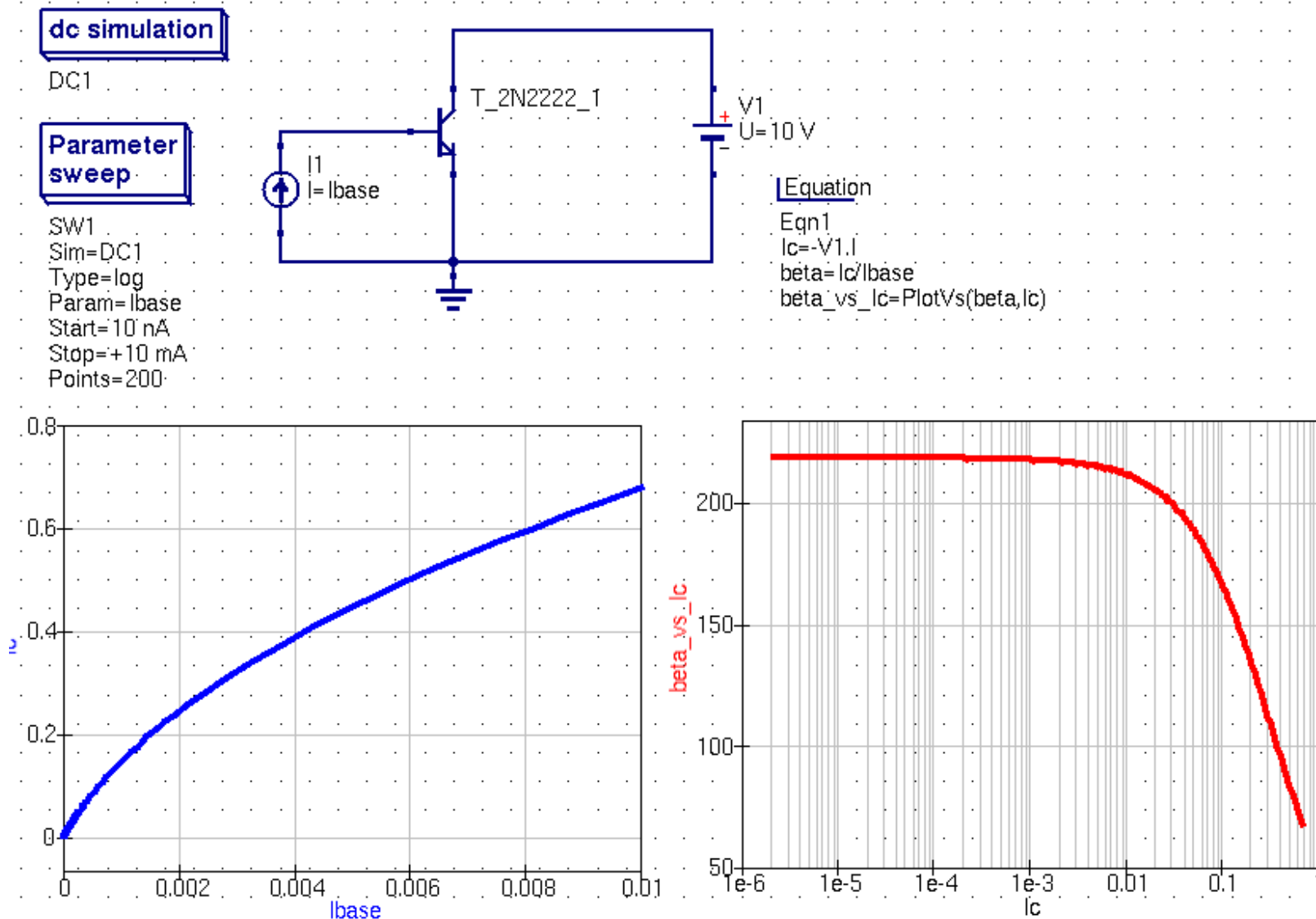
# Quick getting started with Qucs

- Parameter sweeps – can be also cascaded



# S-Parameter Simulation – Bode Plot (guided)


- This will be more discussed during the RF tutorial

## S parameter simulation

SP1  
Type=log  
Start=100 Hz  
Stop=10 GHz  
Points=20001

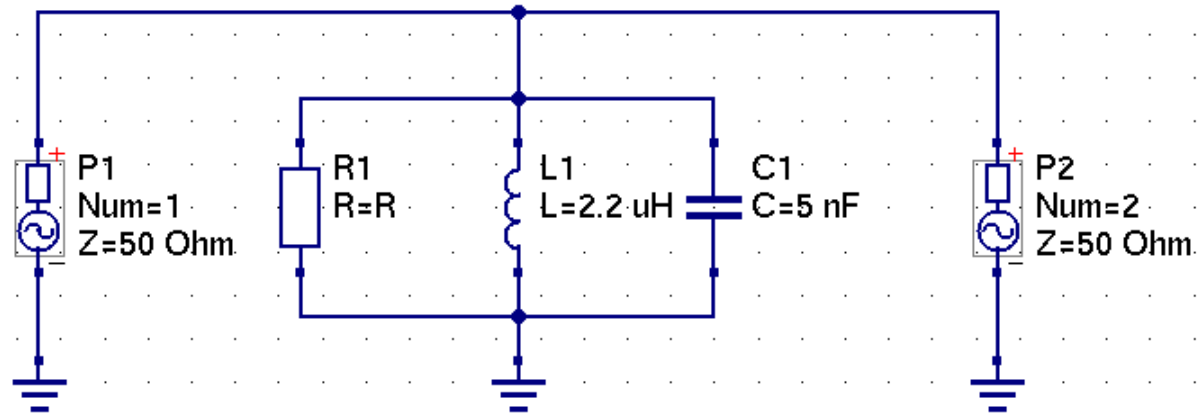
### Equation

Eqn1  
magnitude=S[2,1]  
transmission=dB(S[2,1])  
phase=phase(S[2,1])



### Equation

Eqn2  
R=1000

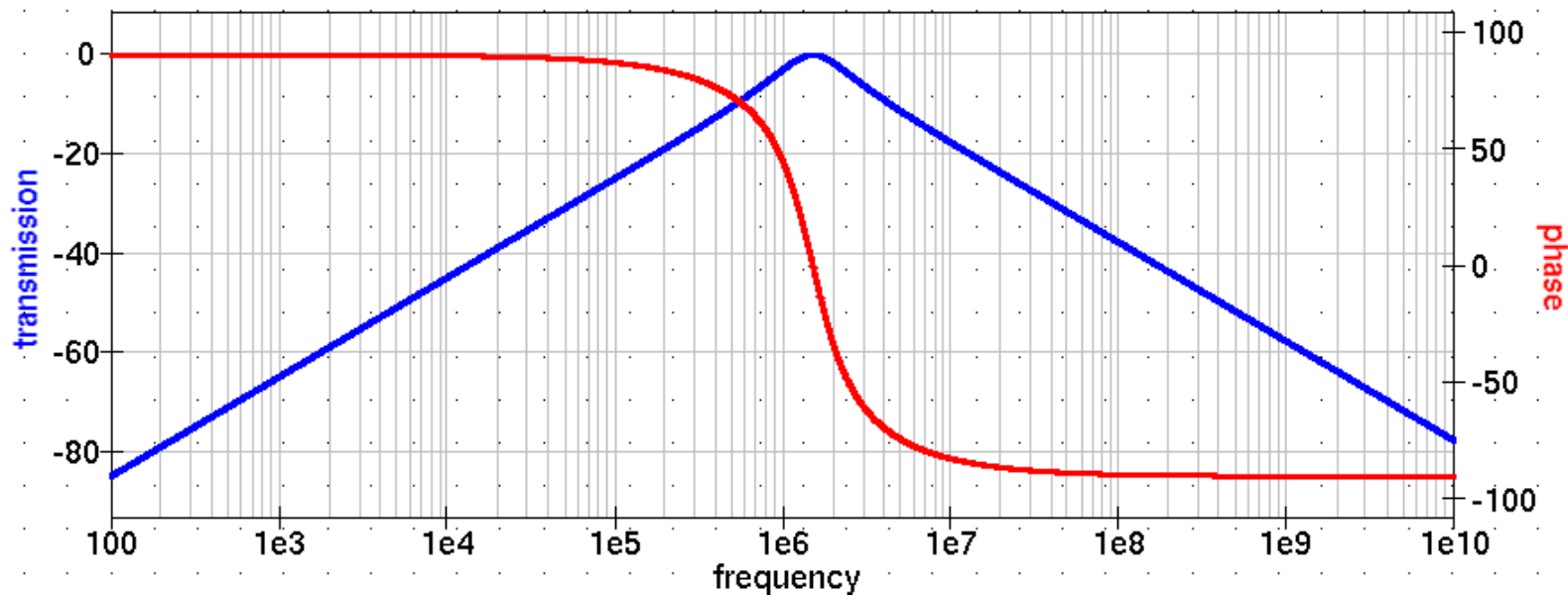

# Exercises – your turn

---

---




# Exercise I

- Get acquainted with Qucs – Repeat the examples for the RC and RL high- and low-pass filters
  - Simulate and plot the transient response.
  - Simulate and plot (Bode) the frequency response
  - Can you make a band-pass out of R, C, and Ls?
  - Discuss the results


**transient  
simulation**

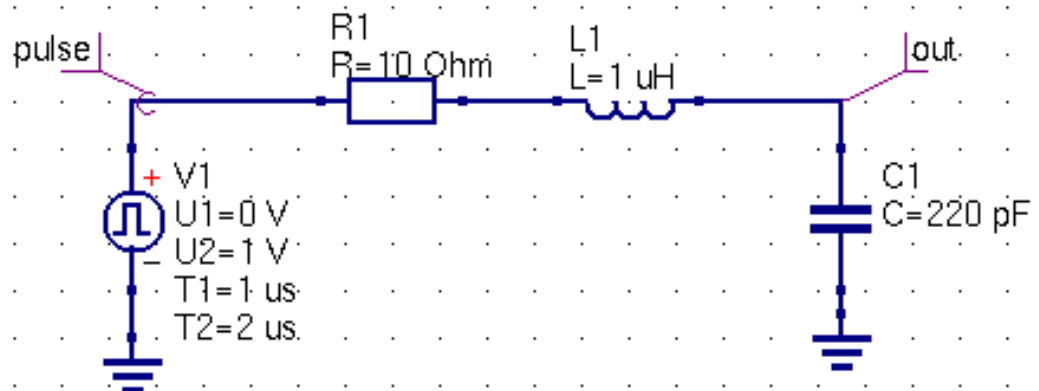TR1  
Type=lin  
Start=0  
Stop=3 us  
Points=1001


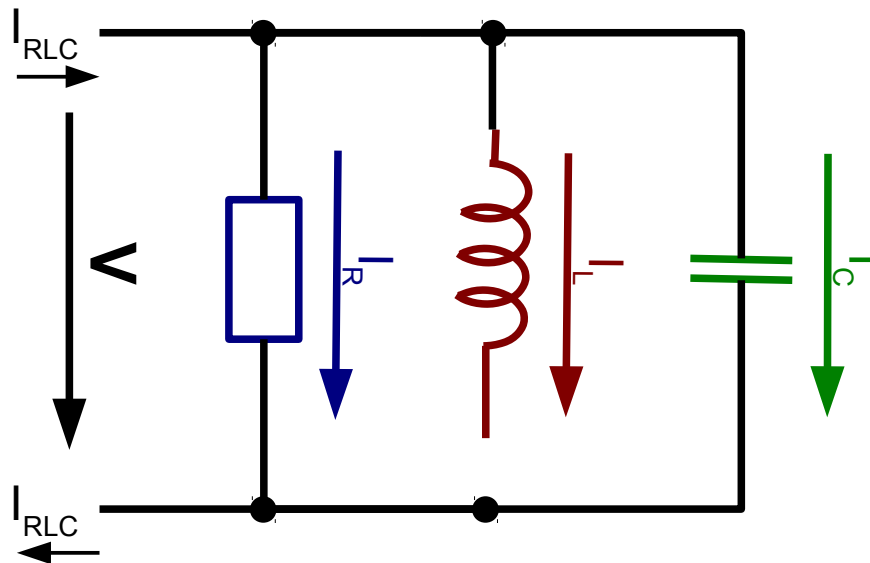
# Exercise II

- A frequency generator ( $Z_i = 50 \Omega$ ) is connected to a lossy LC resonator.
  - N.B. This type of structure is important for discussing cavities, impedances and beam instabilities.
  - a) You have seen the magnitude response for the circuit. Derive the corresponding phase response as a function of  $\omega$ ,  $\omega_0$ , and  $\zeta$ .
  - “Construct“ a parallel RLC resonance circuit schematic with  $L=2.2 \mu\text{H}$ ,  $C=5 \text{ nF}$ , and  $R$  being variable (N.B. use 'Parameter Sweep')..
  - a) Calculate the resonance frequency for  $R = 0\Omega$ .
  - b) Plot and calculate the quality factor  $Q$  for  $R = 0.1, 1, 2, 10, 20, \dots\Omega$  (N.B. use 'Parameter Sweep').
  - c) Discuss the results.



# Exercise III

---

---

- We want to study minute 'betatron motion'\* at the Australian Synchrotron (circumference  $\approx 216$  m).
  - Construct a notch filter that suppresses the first revolution lines and main RF frequency (assume:  $f_{\text{RF}} = 500$  MHz) using only passive components. N.B. There is more than one option!
  - Find the optimal values that would do the job.
    - Somebody mentioned to you that most components are only available for a limited number of values. Find the canonical component values that would match your ideal filter response best.
    - Compare your solution with the real-world R, L, C components including the discussed parasitics.
  - Discuss the pro's, con's and limitations of your solution.

\*These are small transverse oscillations of the electron bunches as they circulate around the machine.



# Exercise IV – Optional

---

---

- Re-use your RLC resonant circuit from exercise II.
  - a) Simulate the transient response to an AC source operating at the LC resonance frequency, and while being
    - switched-on (let the transient stabilise), and
    - subsequently switched-off.
  - b) What are your observations when you increase or decrease the quality factor of the resonance?
    - What impact might this have on e.g. bunch-by-bunch diagnostics?